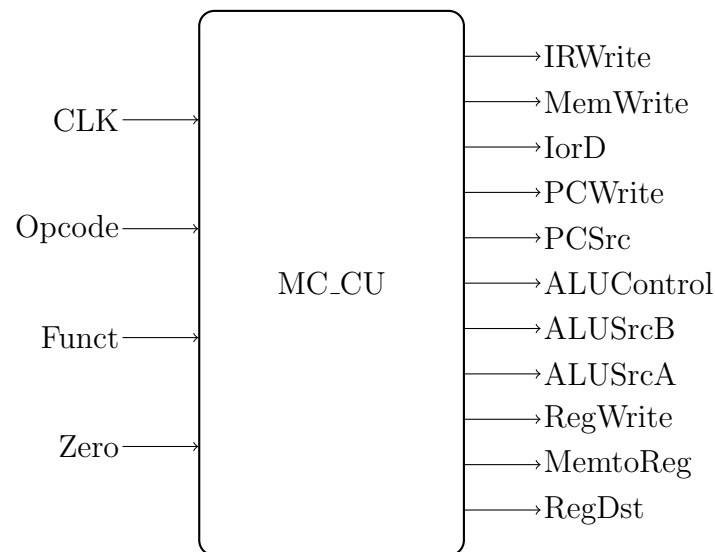


## Multicycle Control Unit

Your task is to program the behavior of an entity called “MC\_CU”. This entity is declared in the attached file “MC\_CU.vhdl” and has the following properties:


- Input: CLK with type `std_logic`
- Input: Opcode with type `std_logic_vector` of length 6
- Input: Funct with type `std_logic_vector` of length 6
- Input: Zero with type `std_logic`
- Output: PCSrc with type `std_logic_vector` of length 2
- Output: ALUControl with type `std_logic_vector` of length 3
- Output: ALUSrcB with type `std_logic_vector` of length 2
- Outputs: IRWrite, MemWrite, IorD, PCWrite, ALUSrcA, RegWrite, MemtoReg, RegDst with type `std_logic`



Do not change the file “MC\_CU.vhdl”.

You will have to implement the following types of instructions:

## R-type:

 

With the opcode representing the instruction, rs and rt the source registers and rd the destination register and funct representing a function for the ALU. The R-type instruction processes the two source registers in the ALU. The ALU result is saved in the destination register specified by rd.

Before the execution of an instruction the instruction has to be fetched and decoded. This takes two clock cycles. During the fetch clock cycle the instruction is read from the current program counter value (PC) and is saved to the instruction register. Also during the fetch clock cycle the PC register is incremented by 4 using the ALU. The next clock cycle is used to decode the instruction in the control unit.

The “MC\_CU” entity shall control the multicycle processor depicted in Figure 1 to perform the following instructions:

instruction	opcode	funct	type
or	000000	100101	R
nor	000000	100111	R

### or

This instruction performs an ALU operation with two register values and saves the result to a register. It takes two clock cycles. First the registers specified in rs and rt are loaded into the ALU and the ALU is sent the or control signal. The ALUControl signal for or can be found in Table 1. In the next clock cycle the ALU Result is saved into the register specified by rd.

### nor

This instruction performs an ALU operation with two register values and saves the result to a register. It takes two clock cycles. First the registers specified in rs and rt are loaded into the ALU and the ALU is sent the nor control signal. The ALUControl signal for nor can be found in Table 1. In the next clock cycle the ALU Result is saved into the register specified by rd.

To get a better understanding of the control signals, here is a description of each control signal. Use Figure 1 to see how the control signals control the data paths.

ALUControl	Function
000	add
101	or
111	nor

Table 1: ALUControls

- IRWrite: When IRWrite is set to ‘1’ then the instruction read from instruction memory gets written to the instruction register, at a rising edge of the CLK signal.
- MemWrite: When MemWrite is set to ‘1’ then the data memory input write data is written to the data memory input address, at a rising edge of the CLK signal.
- IorD: Selects whether the data memory input address comes from the program counter register or from the ALU Result register.
- PCWrite: When PCWrite is set to ‘1’ then the program counter register is written, at a rising edge of the clock signal.
- PCSrc: Selects whether the new program counter value shall come from the ALU, the ALU Result register or the jump address.
- ALUControl: Selects the ALU operation the ALU performs on its two input values. The controls for the available operations are listed in Table 1.
- ALUSrcB: Selects whether the ALU gets a value from the registers read data 2 output, from a constant value of 4, from the sign extended immediate value of the instruction or from the sign extended immediate value of the instruction shifted left by 2 bits.
- ALUSrcA: Selects whether the ALU gets a value from the registers read data 1 output or from the program counter register.
- RegWrite: When RegWrite is set to ‘1’ then the registers write data input is written to the register specified by the write register input, at a rising edge of the clock signal.
- MemtoReg: Selects whether the write data for the registers comes from data memory or from the ALU Result register.
- RegDst: Selects whether the write register input for the registers comes from bits 20 – 16 of the instruction or from bits 15 – 11 of the instruction.

Consider which actions each part of the processor in Figure 1 has to take to fulfill the functions of the operations and set the control signals accordingly. This behavior has to be programmed in the attached file “MC\_CU\_beh.vhdl”.

To turn in your solution write an email to [vhdl-dis+e384@tuwien.ac.at](mailto:vhdl-dis+e384@tuwien.ac.at) with Subject “Result Task 8” and attach your behavior file “MC\_CU\_beh.vhdl”

Good Luck and May the Force be with you.

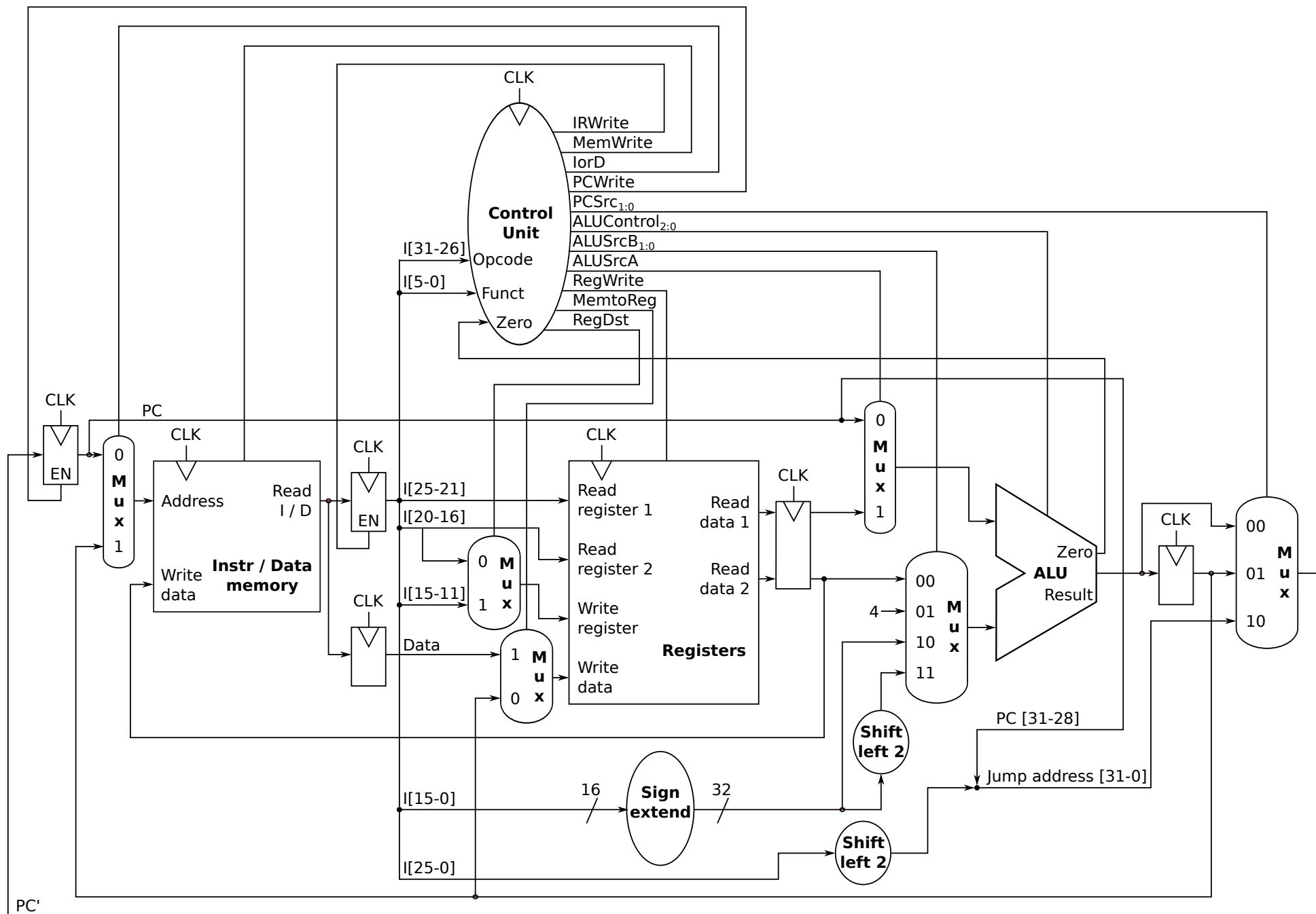


Figure 1: Multicycle processor