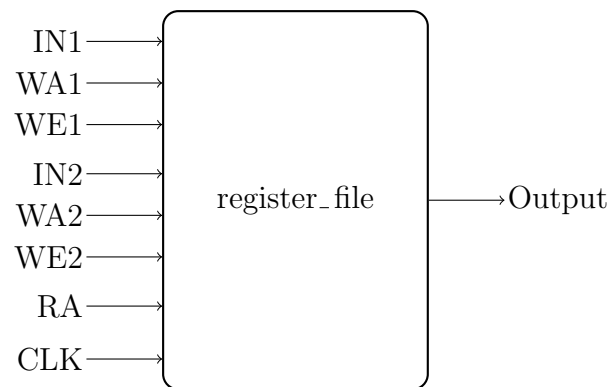


## Register File

Your task is to program the behavior of an entity called “register\_file”. This entity is declared in the attached file “register\_file.vhdl” and has the following properties:

- Input: IN1 with type std\_logic\_vector of length 16
- Input: WA1 and RA with type std\_logic\_vector of length 3
- Input: WA2 with type std\_logic\_vector of length 2
- Input: WE1, WE2 and IN2 with type std\_logic
- Input: CLK with type std\_logic
- Output: Output with type std\_logic\_vector of length 16



Do not change the file “register\_file.vhdl”.

The “register\_file” entity shall contain 7 registers which have to be 16 bit wide each. The input data for registers 1 to 6 comes from the input IN1 and is written to the register specified by the write address WA1 only if the write enable bit WE1 is set to ‘1’. The write address WA2 is used to access the lower 4 bits of the register 0 separately. The input data for the register 0 comes from the input IN2 and shall only be written if the write enable bit WE2 is ‘1’. The output of the entity is the content of a register selected by the read address RA. See Figure 1 for a structural representation of this register file.

Changes of input signals shall become effective at a rising edge of the input CLK signal.

In a situation when the write address WA1 is identical with the read address RA1, then the currently input data IN1 shall be passed through at the next rising edge of the input CLK signal to the Output. This also goes for the special register 0: if a simultaneous read and write from this register occurs, then the input data IN2 shall be also passed through at the next rising edge of the input CLK signal to the Output.

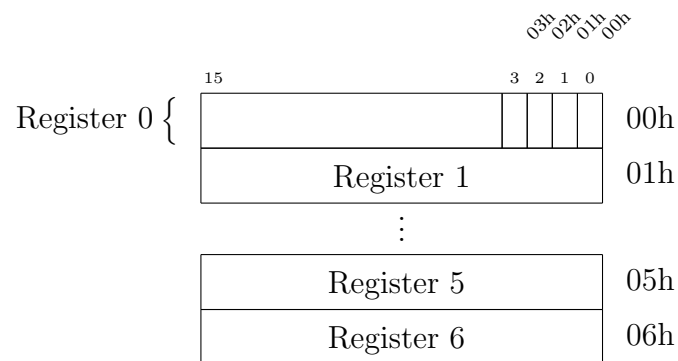


Figure 1: The layout of the register file. Addresses are given as a hexadecimal representation of the binary value.

This behavior, described above, has to be programmed in the attached file “register\_file\_beh.vhdl”.

To turn in your solution write an email to [vhdl-dis+e384@tuwien.ac.at](mailto:vhdl-dis+e384@tuwien.ac.at) with Subject “Result Task 4” and attach your file “register\_file\_beh.vhdl”.

Good Luck and May the Force be with you.